



Computer Organization

COMP2120

Qi Zhao

January 17, 2024

Digital Logic



Boolean Algebra

- Proposed by George Boole in 1854
- Variables: the values of the variables are the truth values true (1) and false (0)
- A Boolean function with k input variables

$$f : \{0, 1\}^k \longrightarrow \{0, 1\} \quad (1)$$

- Operations: **AND** ($A \cdot B$) , **OR** ($A + B$), **NOT** (\bar{A})



Boolean Algebra

- Proposed by George Boole in 1854
- Variables: the values of the variables are the truth values true (1) and false (0)
- A Boolean function with k input variables

$$f : \{0, 1\}^k \longrightarrow \{0, 1\} \quad (1)$$

- Operations: **AND** ($A \cdot B$), **OR** ($A + B$), **NOT** (\bar{A})
- Truth table

| | | A | NOT A |
|---|---|---------|--------|
| | | 0 | 1 |
| | | 1 | 0 |
| A | B | A AND B | A OR B |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}$, $\overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws
 1. Commutative Law

$$AB = BA, A + B = B + A$$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws

1. Commutative Law

$$AB = BA, A + B = B + A$$

2. Identity elements

$$1 \cdot A = A, 0 + A = A$$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws

1. Commutative Law

$$AB = BA, A + B = B + A$$

2. Identity elements

$$1 \cdot A = A, 0 + A = A$$

3. Null law:

$$0 \cdot A = 0, 1 + A = 1$$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws

1. Commutative Law

$$AB = BA, A + B = B + A$$

2. Identity elements

$$1 \cdot A = A, 0 + A = A$$

3. Null law:

$$0 \cdot A = 0, 1 + A = 1$$

4. Idempotent law:

$$A \cdot A = A, A + A = A$$



Boolean Algebra

- **NAND** and **NOR** : the complement (NOT) of AND and OR, $\overline{A \cdot B}, \overline{A + B}$
- **XOR**: exactly one of the operands has the value 1, $A \oplus B$
- Boolean Algebra Laws

1. Commutative Law

$$AB = BA, A + B = B + A$$

2. Identity elements

$$1 \cdot A = A, 0 + A = A$$

3. Null law:

$$0 \cdot A = 0, 1 + A = 1$$

4. Idempotent law:

$$A \cdot A = A, A + A = A$$

5. Inverse law:

$$A \cdot \bar{A} = 0, A + \bar{A} = 1$$



Boolean Algebra

6. Associative law

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C,$$

$$A + (B + C) = (A + B) + C$$



Boolean Algebra

6. Associative law

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C,$$

$$A + (B + C) = (A + B) + C$$

7. Distributive Law

$$A(B + C) = AB + AC$$

$$A + (BC) = (A + B)(A + C)$$



Boolean Algebra

6. Associative law

$$\begin{aligned}A \cdot (B \cdot C) &= (A \cdot B) \cdot C, \\A + (B + C) &= (A + B) + C\end{aligned}$$

7. Distributive Law

$$\begin{aligned}A(B + C) &= AB + AC \\A + (BC) &= (A + B)(A + C)\end{aligned}$$

Proof

$$\begin{aligned}RHS &= (A + B)(A + C) \\&= A \cdot A + A \cdot C + B \cdot A + B \cdot C \\&\text{if } A = 0, RHS = 0 + B \cdot C \\&\text{if } A = 1, RHS = 1 + B + C + B \cdot C = 1 + B \cdot C\end{aligned}$$



Boolean Algebra

8. DeMorgan's Theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B}, \quad \overline{A + B} = \overline{A} \cdot \overline{B}$$



Boolean Algebra

8. DeMorgan's Theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B}, \quad \overline{A + B} = \overline{A} \cdot \overline{B}$$

- Represent Boolean function via Venn diagrams

| Boolean | Sets |
|-------------|---------------------------|
| $A \cdot B$ | $A \cap B$, intersection |
| $A + B$ | $A \cup B$, union |





Boolean Algebra

  8. DeMorgan's Theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B}, \quad \overline{A + B} = \overline{A} \cdot \overline{B}$$




- Represent Boolean function via Venn diagrams




| Boolean | Sets |
|-------------|---------------------------|
| $A \cdot B$ | $A \cap B$, intersection |
| $A + B$ | $A \cup B$, union |



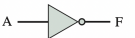

Gates
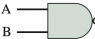
| Name | Graphical Symbol | Algebraic Function | Truth Table | | | | | | | | | | | | | | | |
|------|---|--------------------------------------|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| AND |  | $F = A \cdot B$ or $F = AB$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | |
| OR |  | $F = A + B$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | | | | | | | | |
| NOT |  | $F = \overline{A}$ or $F = A'$ | <table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table> | A | F | 0 | 1 | 1 | 0 | | | | | | | | | |
| A | F | | | | | | | | | | | | | | | | | |
| 0 | 1 | | | | | | | | | | | | | | | | | |
| 1 | 0 | | | | | | | | | | | | | | | | | |

| NAND |  | $F = \overline{AB}$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
|------|---|------------------------|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |
| NOR |  | $F = \overline{A + B}$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |
| XOR |  | $F = A \oplus B$ | <table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | A | B | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| A | B | F | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | | | | | | | | |



Functionally complete sets

- AND, OR, NOT
- AND, NOT: DeMorgan's theorem

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

- OR, NOT, think about it!
- NAND
- NOR

three basic functions can be reduced to **NAND** or **NOR**. Why??



Functionally complete sets

- AND, OR, NOT can be implemented by NAND or NOR

 


Figure 11.2 Some Uses of NAND Gates

- DeMorgan's law, $A + B = \overline{\overline{A} \cdot \overline{B}}$



Functionally complete sets

- DeMorgan's law, $A \cdot B = \overline{\overline{A} + \overline{B}}$.

 


Figure 11.3 Some Uses of NOR Gates



Implementation of Boolean function

Table 11.3 A Boolean Function of Three Variables

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

(b) Boolean Operators Extended to More than Two Inputs (A, B, ...)

| Operation | Expression | Output = 1 if |
|-----------|------------------------------------|---|
| AND | $A \cdot B \cdot \dots$ | All of the set {A, B, ...} are 1. |
| OR | $A + B + \dots$ | Any of the set {A, B, ...} are 1. |
| NAND | $\overline{A \cdot B \cdot \dots}$ | Any of the set {A, B, ...} are 0. |
| NOR | $\overline{A + B + \dots}$ | All of the set {A, B, ...} are 0. |
| XOR | $A \oplus B \oplus \dots$ | The set {A, B, ...} contains an odd number of ones. |

- Sum of products (SOP): $F = XXX + XXX + XXX + \dots$
any of input combinations that produce 1 is true.
- Product of sums (POS): $F = XXX \cdot XXX \cdot XXX \dots$



Implementation of Boolean function

- Sum of products (SOP): $F = XXX + XXX + XXX + \dots$
- **Minterm:** the AND (product) of terms consists of exactly one instance of each literal, e.g. ABC .
- For the $OR(+)$ of minterms, all 0's will have no effect on the final outcome (because $0 + x = x$, for any x)
- 1's for minterms cause the output to be 1 ($1 + x = 1$, for any x).
- By collecting all minterms with $F = 1$, any logical expression can be expressed as a sum of minterms (sum-of-products)



Implementation of Boolean function

Table 11.3 A Boolean Function of Three Variables

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

- Minterms with $F = 1$: 3rd, 4th, 7th rows
- If the value of some variable is 1, take the variable without complementing it, e.g., 3rd row, B
- If the value of some variable is 0, take the variable by complementing it, e.g., 3rd row, \bar{A} , \bar{C} .
- $F = \bar{A}\bar{B}\bar{C} + \bar{A}BC + AB\bar{C}$



Implementation of Boolean function

- Product of sums (POS): non of the input combinations that produce 0 (the row with $F = 0$) is true

$$F = \overline{(\overline{A} \overline{B} \overline{C})} \cdot \overline{(\overline{A} \overline{B} C)} \cdot \overline{(A \overline{B} \overline{C})} \cdot \overline{(A \overline{B} C)} \cdot \overline{(A B C)}$$

Generalized DeMorgan's theorem:

$$\overline{(A \cdot B \cdot C)} = \overline{A} + \overline{B} + \overline{C}$$

- Simplified

$$F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$

- We can implement any logic function by sum-of-product implementation or POS.



Graphical Symbol of the implementation

 


Figure 11.4 Sum-of-Products Implementation of Table 11.3



Graphical Symbol of the implementation

 


Figure 11.5 Product-of-Sums
Implementation of Table 11.3



Simplification

- Sum of products (SOP) $F = \overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$



Simplification

- Sum of products (SOP) $F = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$
- Can we do something better? Yes,



Simplification

- Sum of products (SOP) $F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$
- Can we do something better? Yes,
- Idempotent law: $A + A = A$
- Inverse law: $A + \overline{A} = 1$
- Distributive Law: $A(B + C) = AB + AC$



Simplification

- Sum of products (SOP) $F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$
- Can we do something better? Yes,
- Idempotent law: $A + A = A$
- Inverse law: $A + \overline{A} = 1$
- Distributive Law: $A(B + C) = AB + AC$
- $\overline{A}B\overline{C} + \overline{A}BC = \overline{A}B(\overline{C} + C) = \overline{A}B$
 $\overline{A}B\overline{C} + A\overline{B}\overline{C} = (\overline{A} + A)\overline{B}\overline{C} = \overline{B}\overline{C}$





Simplification

- Sum of products (SOP) $F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$
- Can we do something better? Yes,
- Idempotent law: $A + A = A$
- Inverse law: $A + \overline{A} = 1$
- Distributive Law: $A(B + C) = AB + AC$
- $\overline{A}B\overline{C} + \overline{A}BC = \overline{A}B(\overline{C} + C) = \overline{A}B$
- $\overline{A}B\overline{C} + A\overline{B}\overline{C} = (\overline{A} + A)\overline{B}\overline{C} = \overline{B}\overline{C}$
-

$$\begin{aligned} F &= \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} \\ &= (\overline{A}B\overline{C} + \overline{A}BC) + (A\overline{B}\overline{C} + A\overline{B}C) \\ &= \overline{A}B + \overline{B}\overline{C} = B(\overline{A} + \overline{C}) \end{aligned}$$



Logic gate implementation (optional)

 
 


- Logic Gates are implemented using transistors.
- Transistor can be treated as switches, which turns on/off according to the value of input. If input is 1, the transistor is ON, otherwise it is OFF.



Logic gate implementation (optional)

 
 
- NOT gate
- An additional resistor: protect transistors





Logic gate implementation




- AND gate

  



Logic gate implementation

- OR gate

   



Multiplexers (Optional)

- The multiplexer connects multiple inputs to a single output. One of the inputs is selected to be passed to the output.

 


Figure 11.12 4-to-1 Multiplexer Representation

Table 11.7 4-to-1 Multiplexer Truth Table

| S2 | S1 | F |
|----|----|----|
| 0 | 0 | D0 |
| 0 | 1 | D1 |
| 1 | 0 | D2 |
| 1 | 1 | D3 |



Flip-Flops (Optional)

- The flip-flop is a bistable device. It exists in one of two states and, in the absence of input, remains in that state. Thus, the flip-flop can function as a 1-bit memory.
- The flip-flop has two outputs, which are always the complements of each other. These are generally labeled Q and \bar{Q} .

 


Figure 11.22 The S-R Latch Implemented with NOR Gates



Summary

- Basic operations of Boolean algebra
- All functions on binary numbers can be treated as logic functions.
- The logic function can then be implemented by SOP or POS
- The logic function can then be represented as either NAND or NOR function.
- How to use transistors to implement logic functions